
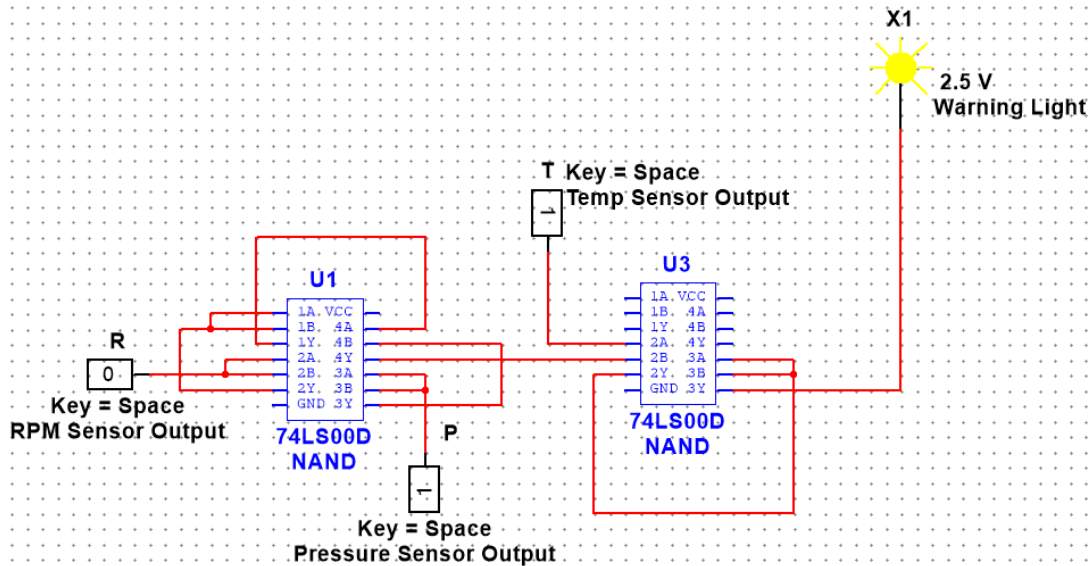




DACD LAB -4

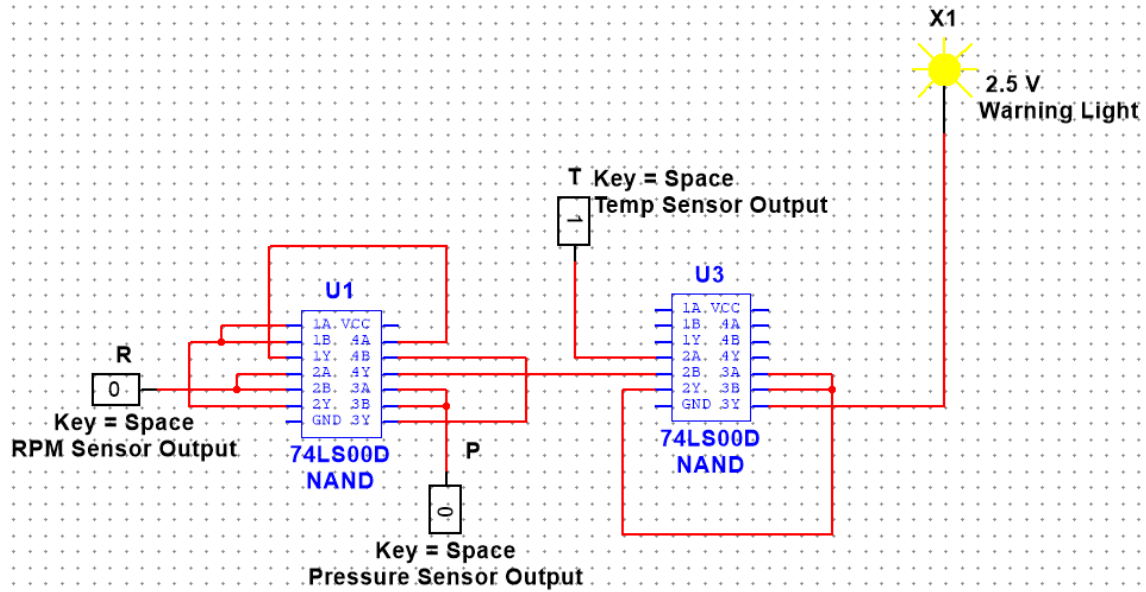1) EQUATION IS $T(P+R')$

Warning light works when $T=1$, and either $P=1$ or $R=0$ or both



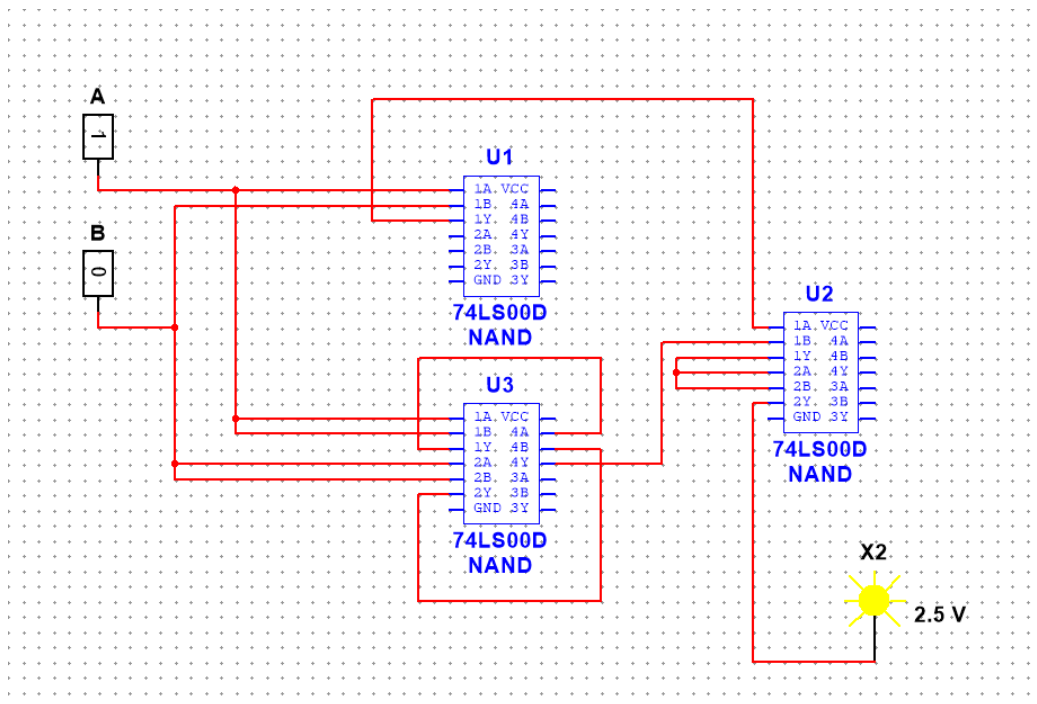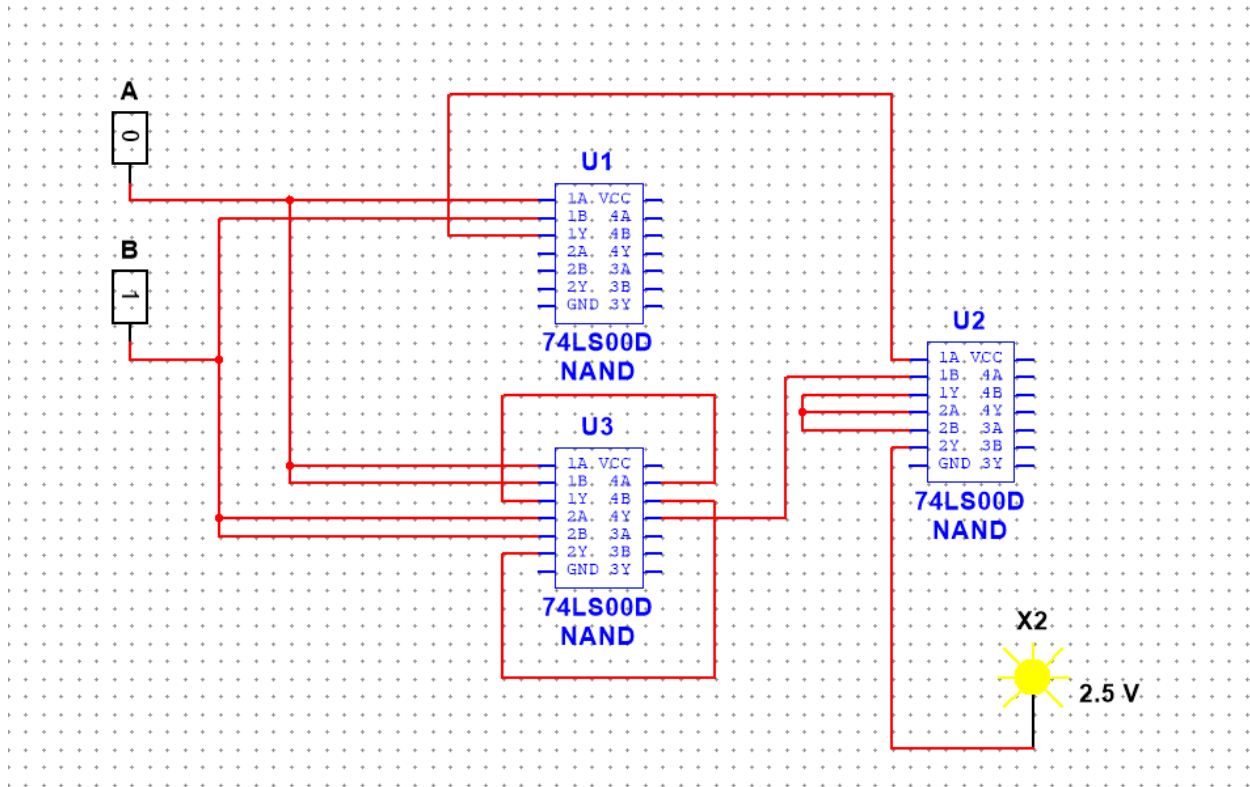- 2) We get the equation as $(AB+A'B)'$ WHICH ON SIMPLIFYING WE GET $(AB)'(A'B)'$.
According to the question when the output is 0 bulb will glow



3)

